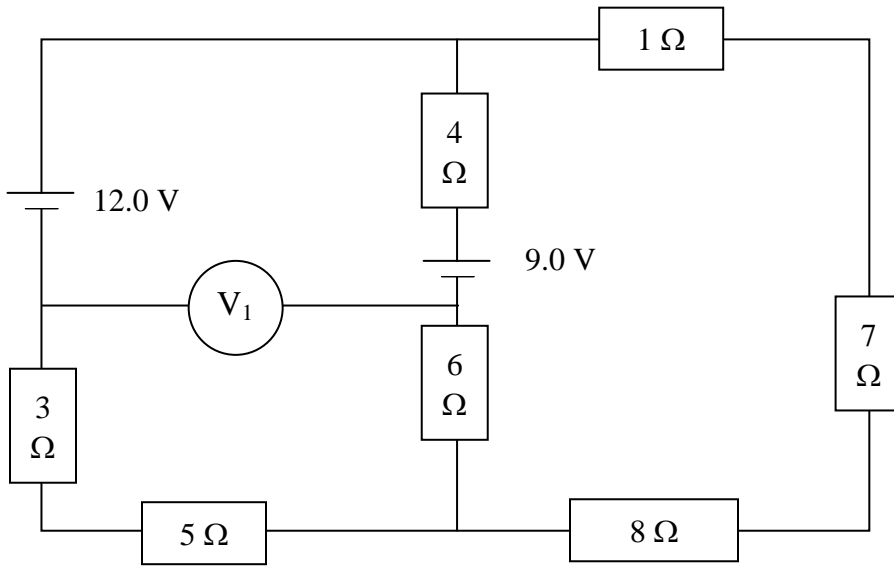


Group Work for 18L

Name _____

1



Find the current and direction (up or down) through:

3 Ω _____

6 Ω _____

7 Ω _____

Find the voltage across:

6 Ω _____

8 Ω _____

Find power dissipated by:

1 Ω _____


4 Ω _____

Find:

$|V_1| =$ _____

I	3	0.457 A	Up
I	6	0.0652 A	Up
I	7	0.522 A	Down
V	6	0.391 V	
V	8	4.174 V	
P	1	0.272 W	
P	4	0.0170 W	
	V1	3.2609 V	

2

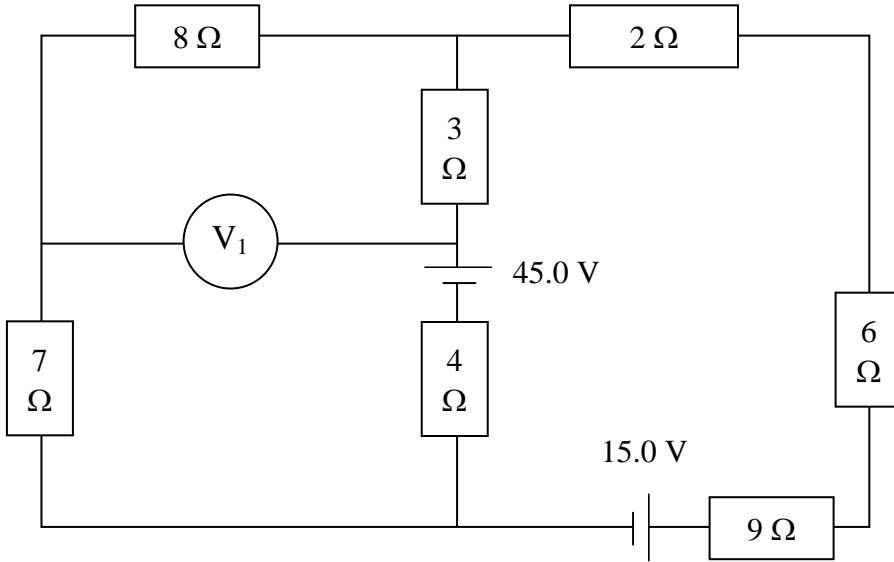

Find the current and direction (up, down) through:

7 Ω _____

4 Ω _____

6 Ω _____

Find the voltage across:

8 Ω _____

2 Ω _____

Find power dissipated by:

3 Ω _____


9 Ω _____

Find:

|V₁| = _____

I	7	1.82 A	Down
I	4	2.54 A	Up
I	6	0.720 A	Down
V	8	14.5 V	
V	2	1.44 V	
P	3	19.3 W	
P	9	4.67 W	
	V ₁	22.1 V	

3

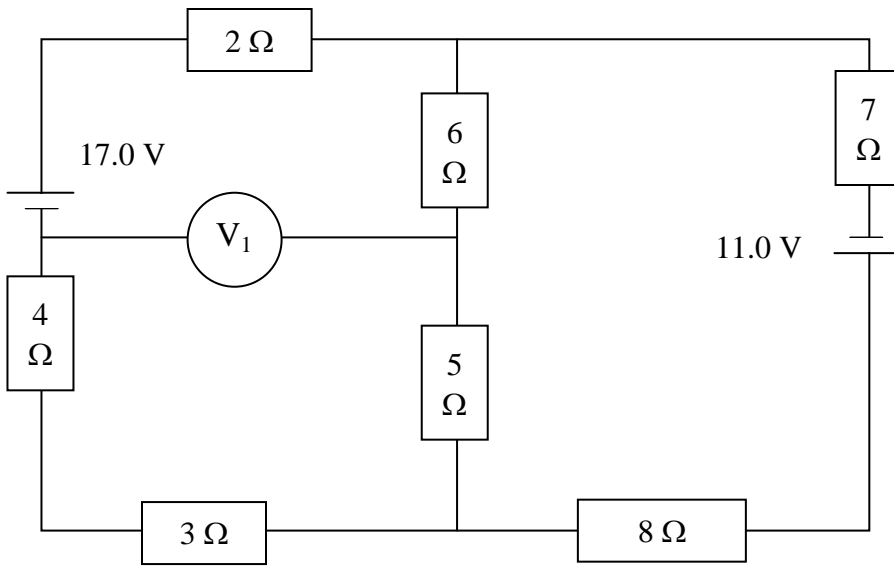

Find the current and direction (up or down) through:

4 Ω _____

5 Ω _____

7 Ω _____

Find the voltage across:

6 Ω _____

8 Ω _____

Find power dissipated by:

2 Ω _____


7 Ω _____

Find:

$|V_1| =$ _____

I	4	1.41 A	Up
I	5	0.391 A	Down
I	7	1.02 A	Down
V	6	2.35 V	
V	8	8.16 V	
P	2	3.98 W	
P	7	7.28 W	
	$ V_1 $	11.832 V	

4

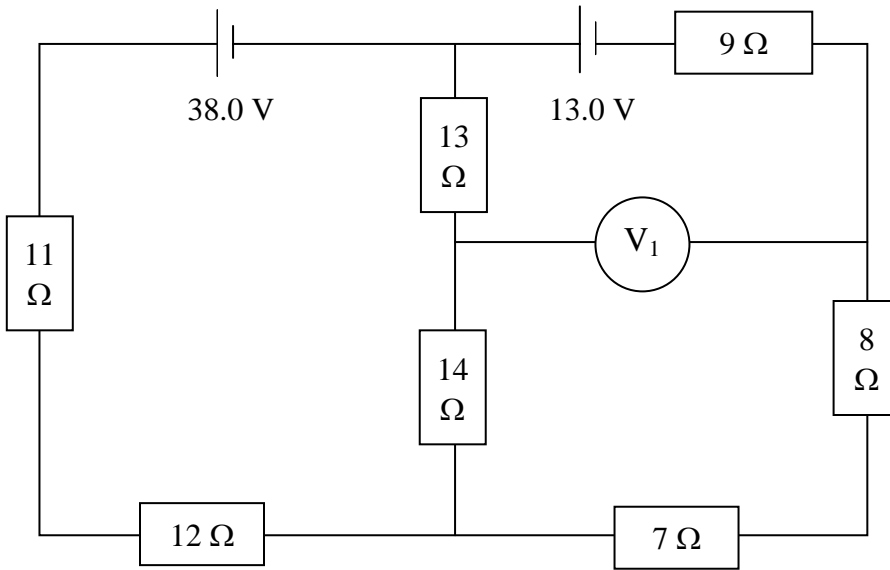

Find the current and direction (up, down, left, right) through:

11 Ω _____

14 Ω _____

8 Ω _____

Find the voltage across:

13 Ω _____

9 Ω _____

Find power dissipated by:

12 Ω _____

7 Ω _____

Find:

$|V_1| =$ _____

I	11	1.26 A	Down
I	14	0.337 A	Up
I	8	0.920 A	Up
V	13	4.38 V	
V	9	8.28 V	
P	12	18.96 W	
P	7	5.93 W	
	$ V_1 $	9.09 V	